



Ch 18 problems

1) 3 nodes

5) D & E, A & B, B & C, C & D, D & E,

A & C, C & E

C is in parallel?

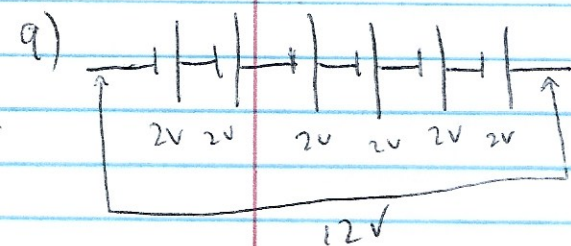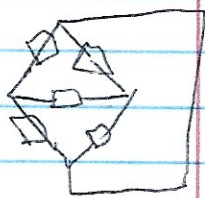

13) $C = \frac{Q}{V}$ $Q = CV = (15 \times 10^{-12} \text{ F})(150 \text{ V})$

$= 2.25 \times 10^{-11} \text{ C}$

17) $C = \epsilon_0 \frac{A}{d} = \epsilon_0 \frac{\pi R^2}{nR}$

If R is doubled, A increases


C changes by a factor of 2

21) (C)

$C = \frac{ab}{(b-a)k}$

25) $C_{eq} = \left(\frac{1}{20 \mu\text{F}} + \frac{1}{30 \mu\text{F}} + \frac{1}{40 \mu\text{F}} \right)^{-1}$

$= 0.012 \mu\text{F}$

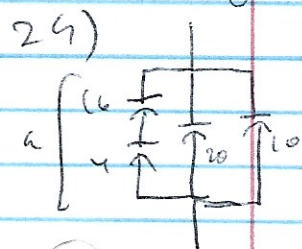

$C_a = \left(\frac{1}{4 \mu\text{F}} + \frac{1}{16 \mu\text{F}} \right)^{-1}$
 $= 3.2 \mu\text{F}$

$C_{eq} = C_a + C_b + C_c$

$= 33.2 \mu\text{F}$


33) a) $Q = CV = (10 \times 10^{-12} \text{ F})(150 \text{ V})$
 $= 1.5 \times 10^{-9} \text{ C}$

b) in parallel c) $Q = CV$

$C = \frac{Q}{V} = \frac{1.0 \text{ C}}{120 \text{ V}} = 8.33 \times 10^{-3} \text{ F}$

$\frac{8.33 \times 10^{-3} \text{ F}}{10 \times 10^{-12} \text{ F}} = 8.33 \times 10^8$ 10 μF capacitors in parallel

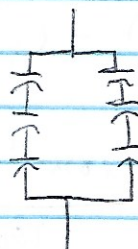37) $\left(\frac{1}{15} + \frac{1}{15} + \frac{1}{15} \right)^{-1} = 5$



all $15 \mu\text{F}$


$C_{eq} = 10 \mu\text{F}$

41) $C = QV$ $PE_c = \frac{1}{2} CV^2$

$C = \frac{2PE_c}{V^2} = \frac{2(1.0 \text{ J})}{(120 \text{ V})^2}$

$= 1.39 \times 10^{-4} \text{ F}$

45)

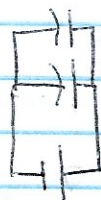

Because C_{eq} is the greatest and the

capacitors are in parallel

49) $PE_c = \frac{1}{2} CV^2$

$C = KC_0$ $\frac{K}{K_{air}} \approx K$

PE_c increases by a factor of K

$$53) C_0 = \frac{\epsilon_0 A}{d} \quad C = \frac{K \epsilon_0 A}{d}$$

$K = \frac{\epsilon}{\epsilon_0}$ equiv. to two capacitors in parallel?

$$C_1 = \frac{K_1 \epsilon_0 (\frac{1}{2} A)}{d} = \frac{K_1 \epsilon_0 A}{2d}$$

$$C_2 = \frac{K_2 \epsilon_0 (\frac{1}{2} A)}{d} = \frac{K_2 \epsilon_0 A}{2d}$$

$$C_{\text{total}} = \frac{(K_1 + K_2) (\epsilon_0 A)}{2d} = C_1 + C_2$$

$$57) C = \frac{Q}{V} = \frac{K \epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ F/m}) (25 \times 10^{-4} \text{ m}^2)}{2000 \text{ m}} \\ = \boxed{1.11 \times 10^{-7} \text{ F}}$$

$$\text{Mean } E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

$$Q = E \epsilon_0 A = (3.0 \times 10^6 \text{ V/m}) (8.85 \times 10^{-12} \text{ F/m}) (25 \times 10^{-4} \text{ m}^2) \\ = 26.6 \text{ C}$$

$$PE = \frac{1}{2} QV = \frac{1}{2} (26.6 \text{ C}) (3.0 \times 10^6 \text{ V})$$

$$= \boxed{3.99 \times 10^7 \text{ J}}$$